

UM–SJTU JOINT INSTITUTE

VE370 - Introduction to Computer Organization
Project 2 Report

Group	32
Name	ID
Han Liying	517370910069
Gracia Stefani	517370990022
Hu Jiaoyang	517370910140

November 5, 2019

Contents

1 Introduction	2
2 Objective	2
3 Single Cycle Implementation	2
3.1 Top Level Diagram	2
3.2 Modules Design	3
3.2.1 Components Design	4
3.2.2 Top Module Design	14
3.3 Simulation	16
3.3.1 Simulation Scenario	16
3.3.2 Textual Result	17
4 Pipelined Implementation	18
4.1 Top Level Diagram	18
4.2 Modules Design	23
4.2.1 Components Design	23
4.2.2 Data Hazards Handling	24
4.2.3 Top Module Design	32
4.3 Simulation	37
4.3.1 Simulation Scenario	37
4.3.2 Textual Result	39
4.4 FPGA Board Implementation	43
5 Conclusion & Discussion	47
6 References	47
7 Appendix	47
7.1 Single Cycle Implementation	47
7.1.1 Source Codes	47
7.1.2 Single Cycle Implementation Textual Result	57
7.2 Pipelined Implementation	70
7.2.1 Source Codes	70
7.2.2 Pipelined Implementation Textual Result	91
7.2.3 Source Codes for FPGA Board Implementation	112

1 Introduction

MIPS structure is commonly seen to implement the processor of computers. In this course VE370, Introduction to Computer Organization, we have learned a lot of instructions supported by MIPS structure, and also the fundamental hardware structure to support those instructions. In this project, we will design the hardware structure to support several MIPS instructions. We will model and simulate in Verilog HDL, and synthesize by using Xilinx synthesis tool.

2 Objective

Our goal is to model both single cycle and pipelined implementation of MIPS computer in Verilog that support a subset of MIPS instruction set including:

- The memory-reference instructions load word (`lw`) and store word (`sw`).
- The arithmetic-logical instructions `add`, `addi`, `sub`, `and`, `andi`, `or`, and `slt`.
- The jumping instructions branch equal (`beq`), branch not equal (`bne`), and jump (`j`),

For single cycle implementation, we will mainly design and use 11 modules, which are modules for PC, Mux, Adder, ALU, ALU Control, Control, Register File, Instruction Memory, Data Memory, Sign Extension, and Shift Left. We write testbenches to simulate our single cycle implementation.

For pipelined implementation, we will mainly design and use 14 modules, which are modules for PC, Mux, Adder, ALU, ALU Control, Control, Register File, Instruction Memory, Data Memory, Sign Extension, Shift Left, Hazard Detection, Forwarding Unit, and Pipeline Register. We write testbenches to simulate our pipelined implementation, and then use FPGA board to demonstrate our result by SSD display.

3 Single Cycle Implementation

3.1 Top Level Diagram

Our diagram of top-level block for single cycle implementation is similar to the one shown in Figure [1](#), but we add one more control signal `nBranch` for detecting `bne`, and then add one or gate whose input is `nBranch` and `eBranch` (for `beq`). The output of this or gate is then forwarded to the **Mux module** which selects from branch address or `PC + 4` address. Figure [2](#) shows the schematic generated by **Vivado** software.

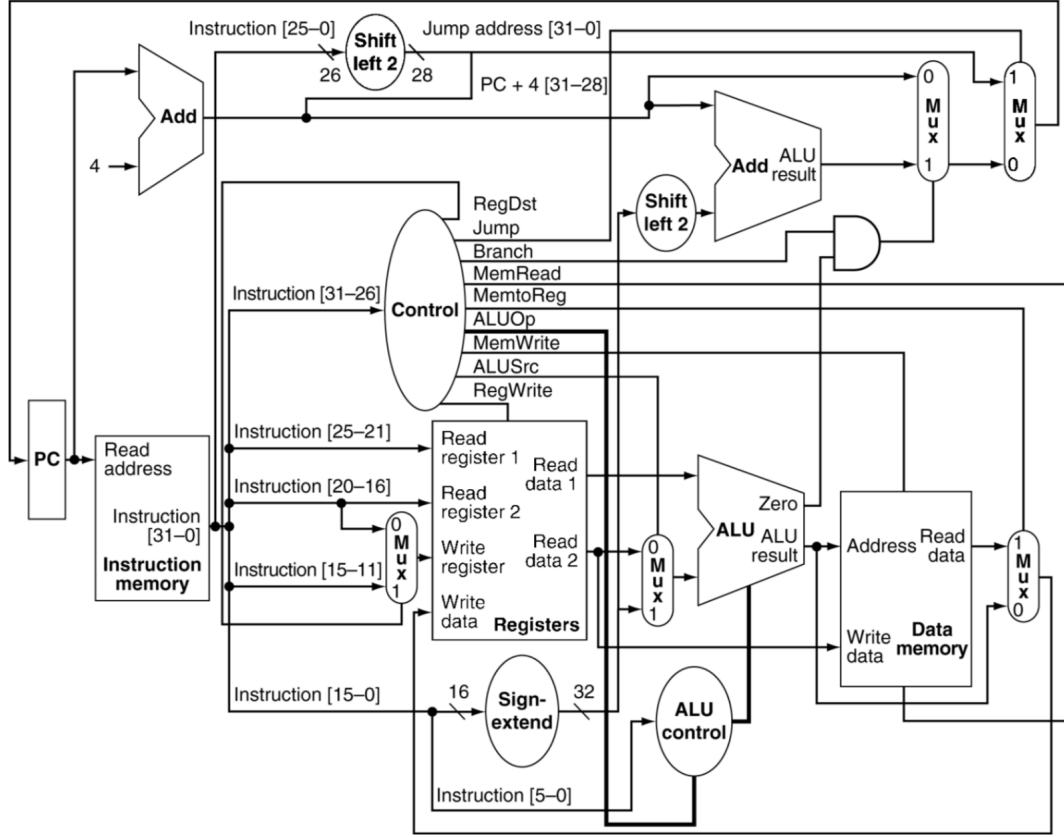


Figure 1: The top-level block diagram for single cycle implementation [1].

 


Figure 2: The schematic diagram for single cycle implementation.

3.2 Modules Design

We mainly need to design and use 11 component modules, which are modules for PC, Mux, Adder, ALU, ALU Control, Control, Register File, Instruction Memory, Data Memory, Sign Extension, and Shift Left. Finally write a main module to combine them together so that we can fulfill the function of single cycle structure.

3.2.1 Components Design

PC module is used to calculate the address of $PC + 4$, we write the module in `pc.v`. The output is `outAddrs`, and input is `pcAddrs`, `clock` and `reset`. At first use we initialize the output of this module to be 0.

```
1 module PC (pcAddrs, clock, outAddrs, reset);
2   input [31:0] pcAddrs;
3   input clock, hold, reset;
4   output [31:0] outAddrs;
5
6   reg [31:0] pcReg;
7
8   initial begin
9     pcReg = 32'b0;
10  end
11
12  always @(negedge clock) begin
13    if(reset == 1'b1) pcReg = 32'b0;
14    else pcReg = pcAddrs;
15  end
16  assign outAddrs = pcReg;
17 endmodule
18 }
```

ALU module is written in `ALU.v`. The ALU has two input ports, `in1` and `in2` which takes in two 32 bits data. It also takes control signal in the `control` port to tell the ALU which operation to execute. The control signal `4'b0000` tells the ALU to do the and operation, `4'b0001` for the or operation, `4'b0010` for the add operation, `4'b0110` for the subtract operation, `4'b0111` for the set-on-less-than operation and `4'b1100` for the nor operation. If the control signal is not recognized by the ALU, it will display "ALU invalid control signal [control]" for the simulation. The Verilog code of the module is as follows:

```
1 module ALU (in1, in2, control, zero, aluRes);
2   input signed [31:0] in1, in2; //Signed input
3   input [3:0] control; //Control signal input telling ALU
4   //Which instruction to execute
5   output [31:0] aluRes; //The result output of the ALU
6   output zero;
7
8   reg [31:0] aluRes;
9   reg zero;
10
11  always @ (*) begin
12    case (control)
```

```

13      4'b0000: aluRes <= in1 & in2; //and
14      4'b0001: aluRes <= in1 | in2; //or
15      4'b0010: aluRes <= in1 + in2; //add
16      4'b0110: aluRes <= in1 - in2; //subtract
17      4'b0111: begin //set-on-less-than
18          if(in1 < in2) begin
19              aluRes <= 32'b1;
20          end
21          else begin
22              aluRes <= 32'b0;
23          end
24      end
25      4'b1100: aluRes <= ~(in1 | in2); //nor
26      default begin
27          \display("ALU_invalid_control_signal_\%b", control);
28      end
29  endcase
30      if (aluRes == 32'b0) zero = 1'b1;
31      else zero = 1'b0;
32  end
33 endmodule

```

Data Memory module is written in `dataMem.v`. The Data Memory module has 5 inputs: `clock`, `memRead`, `memWrite`, `address`, `wData`. The Data Memory module is triggered by the negative edge of the clock such that it will only write to the memory at the negative edge of the clock. It will only write the data `wData` to the memory in the address `address` if `memWrite == 1`. In this design, it will always read from the memory, however the `memRead` signal is used later in the main implementation. It also has a parameter `memWords`, indicating how many words wants to be stored in the memory, which is set to 32 by default. The Data Memory has a private register `dataMem` which can hold up to $4 * \text{memWords}$ of 8-bit data, which means the data memory can store `memWords` words. The data memory is initially cleared to 0. The Verilog code is as follows:

```

1
2 module dataMem(clock, memRead, memWrite, address, wData, rData);
3     input clock, memRead, memWrite;
4     input [31:0] address, wData;
5     output [31:0] rData;
6
7     parameter memWords = 32; //can store 32 32-bits data (32x32 memory)
8     reg [7:0] dataMem [4*memWords - 1:0];
9
10    integer i;

```

```

11 initial begin //clear the memory
12     //rData <= 8'b0; //read data will initially be 0
13     for (i=0; i < 4*memWords; i = i+1) begin
14         dataMem[i] = 8'b0;
15     end
16 end
17
18 assign rData = \{ dataMem[address],
19     dataMem[address+1],
20     dataMem[address+2],
21     dataMem[address+3]\};
22
23 always @(negedge clock) begin
24     if (memWrite == 1'b1) begin
25         \{dataMem[address],
26             dataMem[address+1],
27             dataMem[address+2],
28             dataMem[address+3]\} <= wData;
29         \display("writing_to_dataMem[\%h],_supposed_value_=_0x\%h", address,
30             wData);
31     end
32
33     if (memRead == 1'b1) begin
34         \display("Data_read_from_dataMem[\%h]_=_0x\%h", address, rData);
35     end
36 end
37
38 endmodule

```

ALU control module is written in `ALUcontrol.v`. It receives one input signal `ALUop` from **Control module**, and another input signal `funct` from the lower 6 bits of instruction code. Then the output `ALUsel` is used to control the calculation of **ALU module**. The following code shows how it is implemented:

```

1 module ALUcontrol(ALUop, funct, ALUsel);
2
3     input [1:0] ALUop;    // 2-bit ALUop from opcode
4     input [5:0] funct;    // 5-bit funct from instruction
5     output reg [3:0] ALUsel; // 4-bit output of ALUcontrol unit
6
7     initial begin
8         ALUsel = 4'b0000;    // initialize ALUsel
9     end
10

```

```

11 always @(*) begin
12     if (ALUOp == 2'b00) begin // lw, sw, addi
13         ALUsel <= 4'b0010;
14     end else
15     if (ALUOp == 2'b01) begin // beq, bne
16         ALUsel <= 4'b0110;
17     end else
18     if (ALUOp == 2'b11) begin // andi
19         ALUsel <= 4'b0000;
20     end
21     else if (ALUOp == 2'b10) begin
22         if (funct == 6'b100000) begin //add
23             ALUsel <= 4'b0010;
24         end
25         else if (funct == 6'b100010) begin //subtract
26             ALUsel <= 4'b0110;
27         end
28         else if (funct == 6'b100100) begin //and
29             ALUsel <= 4'b0000;
30         end
31         else if (funct == 6'b100101) begin //or
32             ALUsel <= 4'b0001;
33         end
34         else if (funct == 6'b101010) begin //slt
35             ALUsel <= 4'b0111;
36         end
37     end
38 end
39
40 endmodule

```

Control module is written in Control.v. It receives input signal opcode from the highest 6 bits of instruction code, and then output 10 control signals RegDst, Jump, eBranch, nBranch, MemRead, MemtoReg, ALUOp, ALUSrc, MemWrite, RegWrite. The following code shows how it is implemented:

```

1 // Get control signal from opcode
2 // Support: 'lw', 'sw', 'add', 'addi', 'sub', 'and', 'andi', 'or', 'slt',
3 // 'beq', 'bne', 'j'
4
5 module Control(
6     opcode,           // The opcode we get from insturction.
7     RegDst,           // Determine the destination register to wirte,
8                       // rt or rd.
9     Jump,             // Do 'jump' instruction.

```



```

10     eBranch,          // Do 'beq' instruction.
11     nBranch,          // Do 'bne' instruction
12     MemRead,          // Whether read data from data memory.
13     MemtoReg,         // Which data to write into RF, the output of ALU
14                       // or data read from data memory.
15     ALUOp,            // Get ALUOp from opcode for ALU control unit.
16     ALUSrc,           // Determine the source to use for ALU,
17                       //the data from RF or extended immediate.
18     MemWrite,         // Whether write data into data memory.
19     RegWrite          // Whether write data into RF.
20 );
21
22 input [5:0] opcode;
23 output reg [1:0] ALUOp;
24 output reg RegDst, Jump, eBranch, nBranch, MemRead, MemtoReg, ALUSrc,
    MemWrite, RegWrite;
25
26 initial begin
27     // Initialize
28     Jump = 1'b0;
29     ALUSrc = 1'b0;
30     RegDst = 1'b0;
31     ALUOp = 2'b00;
32     MemWrite = 1'b0;
33     MemRead = 1'b0;
34     eBranch = 1'b0;
35     nBranch = 1'b0;
36     MemtoReg = 1'b0;
37     RegWrite = 1'b0;
38 end
39
40 always @ (*) begin
41     Jump <= 1'b0;
42     ALUSrc <= 1'b0;
43     RegDst <= 1'b0;
44     ALUOp <= 2'b00;
45     MemWrite <= 1'b0;
46     MemRead <= 1'b0;
47     eBranch <= 1'b0;
48     nBranch <= 1'b0;
49     MemtoReg <= 1'b0;
50     RegWrite <= 1'b0;
51     if (opcode == 6'h0) begin // add/and/sub/or/slt
52         RegDst <= 1'b1;
53         ALUOp <= 2'b10;

```

```

54     RegWrite <= 1'b1;
55 end else
56     if (opcode == 6'h8) begin // addi
57         ALUSrc <= 1'b1;
58         ALUOp <= 2'b00;
59         RegWrite <= 1'b1;
60     end else
61     if (opcode == 6'hc) begin // andi
62         ALUSrc <= 1'b1;
63         ALUOp <= 2'b11;
64         RegWrite <= 1'b1;
65     end else
66     if (opcode == 6'h4) begin // beq
67         ALUOp <= 2'b01;
68         eBranch <= 1'b1;
69     end else
70     if (opcode == 6'h5) begin // bne
71         ALUOp <= 2'b01;
72         nBranch <= 1'b1;
73     end else
74     if (opcode == 6'h23) begin // lw
75         ALUSrc <= 1'b1;
76         MemRead <= 1'b1;
77         MemtoReg <= 1'b1;
78         RegWrite <= 1'b1;
79     end else
80     if (opcode == 6'h2b) begin // sw
81         ALUSrc <= 1'b1;
82         MemWrite <= 1'b1;
83     end else
84     if (opcode == 6'h2) begin // j
85         Jump <= 1'b1;
86     end
87 end
88
89 endmodule

```

Register File module is written in RegisterFile.v. It is triggered by clock signal clk, and receives input signal RegWrite from **Control module**. The input signal also includes readRegister1, readRegister2, writeRegister, writeData. Then the output of this module are readData1 and readData2. Only when the RegWrite signal is 1, the register file begins to write data into register file. The following code shows how it is implemented:

```

1 // 32*32 Register File

```

```

2
3 module RegisterFile(
4     clk,                // Clock signal
5     RegWrite,           // Control signal to write
6     readRegister1,      // First register of read
7     readRegister2,      // Second register of read
8     writeRegister,       // Register to write
9     writeData,           // Data to write
10    readData1,           // Data read from the first register
11    readData2            // Data read from the second register
12);
13
14 input clk, RegWrite;
15 input [4:0] readRegister1, readRegister2, writeRegister;
16 input [31:0] writeData;
17 output [31:0] readData1, readData2;
18
19
20 reg [31:0] RegisterFile [0:31];
21 // initialize
22 integer i;
23 initial begin
24     for (i=0; i<32; i=i+1) // initialize the register file
25         RegisterFile[i] = 32'b0;
26 end
27
28 // always read
29 assign readData1 = RegisterFile[readRegister1];
30 assign readData2 = RegisterFile[readRegister2];
31
32 always @ (posedge clk) begin
33     if (RegWrite == 1'b1) begin
34         RegisterFile[writeRegister] <= writeData;
35     end
36 end
37
38 endmodule

```

ShiftLeft is written in `ShiftLeft2.v`. The **ShiftLeft** module has 1 input: `Input`, and 1 output: `ShiftedOutput`. The **ShiftLeft** module is asynchronous, and is activated only when there is input. There are two uses for `shiftright2`, first is in branch instructions where the $address = PC + offset * 4 + 4$, with offset being a 4 digit number. The second usage is in jump instructions, where the 26 digits of immediate is shifted by left 2 to 28 digits, before the top four digits of PC is appended to the address. Since in these two usages, the digits

of the number can be different, we set the digits as a parameter. The Verilog code is as follows:

```
1  module ShiftLeft2(  
2      Input,  
3      ShiftedOutput  
4  );  
5      //by HU Jiaoyang 517370910140 in VE370 Project 2 in 19FA  
6      //There are two uses for shiftright2, first is in branch instructions where  
7      //the address = PC+offset*4+4, with offset being a 4 digit number  
8      //The second usage is in jump instructions, where the 26 digits of immediate  
9      //is shifted by left 2 to 28 digits, before the top four digits of PC is  
10     //appended to the address  
11     parameter ShiftAmount = 2;  
12     parameter Digits = 32; //this is subject to change depending on which path  
13     //this component is on  
14     input [Digits - 1:0] Input;  
15     output [Digits - 1:0] ShiftedOutput;  
16  
17     assign ShiftedOutput = {Input[Digits - 1-ShiftAmount:0], {ShiftAmount{1'b0  
18         }}}; //this instruction takes the lower 30 (could be less 30) digits and  
19     //adds two 00 after the digits,  
20     //which times the digits by 4 and shifts two digits  
21 endmodule
```

SignExtend module is written in SignExtend.v. The SignExtend module has 1 input: Input, and 1 output: Output. The SignExtend module is asynchronous, and is activated only when there is input. The module is normally used in I-type instructions, like branch. This component extends the 16-bit immediate field to 32 full bits to obtain the final address in branch instructions, the extended parts have the same digit as the most significant digit of the input. The Verilog code is as follows:

```
1  module SignExtend(  
2      Input,  
3      Output  
4  );  
5      //by HU Jiaoyang 517370910140 in VE370 Project 2 in 19FA  
6      //This component extends the 16-bit immediate field to 32 full bits to obtain  
7      //the final address in branch instructions, the extended parts have the same  
8      //digit as the most significant digit of the input  
9      parameter Digits = 32;  
10     parameter ImmeDigits = 16;  
11     input [ImmeDigits-1:0] Input;
```

```

10 output [Digits-1:0] Output;
11
12 assign Output = {{(Digits-ImmeDigits){Input[ImmeDigits-1]}}, Input};
13
14 endmodule

```

Instruction Memory module is written in `InstructionMemory.v`. The Instruction Memory module has 1 input: Address, and 1 output: Instruction. The Instruction-Memory module is asynchronous, and is activated only when there is input. This component takes addresses of instructions as input and stores the instruction codes in two dimensional arrays. The module has a private register, which is the memory storing all the instructions. We set the size of a unit of the instruction codes to be 8-digit, because computer instructions are based on 8-bit storage, and size of the memory 256 bits because the Memory needs to be large enough. Inside the codes is a sample instruction memory provided by TAs. The Verilog code is as follows:

```

1  module InstructionMemory(
2      Address,
3      Instruction
4  );
5      //by HU Jiaoyang 517370910140 in VE370 Project 2 in 19FA
6      //This component takes addresses of instructions as input and output the
7          instruction codes
8      input  [31:0] Address;
9      output [31:0] Instruction;
10     reg [7:0] Memory[0:255]; //This is the whole Memory, storing all the
11         instructions. 8 bit because computer instructions are based on 8-bit
12         storage, and 256 bits because the Memory needs to be large enough
13
14     initial $readmemb("Instruction.txt",Memory); //this statement loads up the
15         Memory at simulation time 0 starting at the Memory address 1
16
17     end
18     assign Instruction = {Memory[Address],Memory[Address+1],Memory[Address+2],
19         Memory[Address+3]}; //This is straightforward,each slot stores eight
20         hexadecimal numbers, and we combine four of them to form a complete
21         instruction
22 endmodule

```

Adder module is written in `Adder.v`. The Adder module has 2 inputs: Input1, Input2 to be added, and 1 output: Output. The Adder module is asynchronous, and is activated only when there are inputs. This module is used to compute address for program counter to move on to the next instruction, or to obtain the final address in jump and branch instruc-

tions. The Verilog code is as follows:

```
1  `timescale 1ns/100ps
2  module Adder (
3      Input1,
4      Input2,
5      Output
6  );
7      //by HU Jiaoyang 517370910140 in VE370 Project 2 in 19FA
8      //This is used to compute address for program counter to move on to the next
          instruction, or to obtain the final address in jump and branch
          instructions
9  parameter Digits = 32;
10
11  input [Digits-1:0] Input1,Input2;
12  output [Digits-1:0] Output;
13
14  assign Output = Input1+Input2;
15
16  endmodule
```

Mux module is written in Mux.v . The Mux module has 2 inputs: Input1,Input2 to be selected, and 1 output:Output. The Mux module is asynchronous, and is activated only when there are inputs. This module is used to output input1 or input2 depending on the selection signal, selecting sources for the ALU; or it can select whether to use the data from Data Memory or from registers. The Verilog code is as follows:

```
1  module Mux (
2      Selection,
3      Input1,
4      Input2,
5      Output
6  );
7      //by HU Jiaoyang 517370910140 in VE370 Project 2 in 19FA
8      //this does so much things,it outputs input1 or input2 depending on the
          selection signal, selecting sources for the ALU, selecting whether to use
          the data from DM or from registers...
9  parameter Digits = 32; //this is subject to change depending on which path this
          component is on
10  input [Digits-1:0] Input1,Input2;
11  output reg [Digits-1:0] Output;
12  input Selection;
13
```

```

14 always @ (*) begin
15 if(Selection == 0) begin Output = Input1; end
16 if(Selection == 1) begin Output = Input2; end
17 end
18 endmodule

```

3.2.2 Top Module Design

After completing all necessary modules, we work on the **Top Module** to implement the whole function of single cycle. The structure is the same as the top level diagram shown as Figure 2. This module is written in `main_single.v`.

```

1 `include "ShiftLeft2.v"
2 `include "Mux.v"
3 `include "Adder.v"
4 `include "SignExtend.v"
5 `include "ALUcontrol.v"
6 `include "Control.v"
7 `include "RegisterFile.v"
8 `include "ALU.v"
9 `include "dataMem.v"
10 `include "pc.v"
11 `include "InstructionMemory.v"
12 module main(clk, reset);
13     input clk, reset;
14     wire [31:0] pc_out, add1_out, add2_out, mux2_out, mux3_out, mux4_out,
15         mux5_out, ins_out, signextend_out, reg_read1, reg_read2, ALU_result,
16         dataMem_out, shift2_out, jumpAddress;
17     wire [27:0] shift1_out;
18     wire [25:0] ins_except_op;           // instruction code without opcode
19     wire [15:0] ins_imm;                 // immediate part of instruction
20     wire [5:0] ins_opcode, ins_funcnt; // opcode and funct part of instruction
21     wire [4:0] mux1_out, ins_rs, ins_rt, ins_rd;
22     wire [3:0] ALUsel;
23     wire [1:0] ALUop;
24     wire RegDst, Jump, eBranch, nBranch, MemRead, MemtoReg, MemWrite, ALUSrc,
25         RegWrite, and1_out, and2_out, or_out, ALU_zero, reset;
26
27     reg [31:0] add_amount;
28     //Let the modules initialize on the first clock cycle
29     initial begin add_amount = 32'b0; end
30
31     Adder adder1(pc_out, add_amount, add1_out); // add1 for pc+4.
32     Adder adder2(add1_out, shift2_out, add2_out); // add2 for branch
33     ALU alu(reg_read1, mux2_out, ALUsel, ALU_zero, ALU_result);

```

```

31  ALUcontrol alucontrol(ALUOp, ins_funcnt, ALUsel);
32  dataMem dataMemory(clk, MemRead, MemWrite, ALU_result, reg_read2,
    dataMem_out);
33  InstructionMemory insMem(pc_out, ins_out);
34
35  Control control(ins_opcode, RegDst, Jump, eBranch, nBranch, MemRead,
    MemtoReg, ALUOp, ALUSrc, MemWrite, RegWrite);
36
37  Mux #(.Digits(5))mux1(RegDst, ins_rt, ins_rd, mux1_out);
38  // mux1 for choosing rt or rd
39  Mux mux2(ALUSrc, reg_read2, signextend_out, mux2_out);
40  // mux2 for choosing ALU_b
41  Mux mux3(MemtoReg, ALU_result, dataMem_out, mux3_out);
42  // mux3 for choosing write-back data
43  Mux mux4(or_out, add1_out, add2_out, mux4_out); // mux4 for branch
44  Mux mux5(Jump, mux4_out, jumpAddress, mux5_out); // mux5 for jump
45
46  PC pc (mux5_out, clk, pc_out, reset);
47  RegisterFile regFile(clk, RegWrite, ins_rs, ins_rt, mux1_out, mux3_out,
    reg_read1, reg_read2);
48  ShiftLeft2 shift2(signextend_out, shift2_out); // shift2 for brach address
49  ShiftLeft2 #(.Digits(28)) shift1 ({2'b0, ins_except_op}, shift1_out);
50  // shift1 for jump address
51  SignExtend #(.Digits(32), .ImmeDigits(16)) ext (.Input(ins_imm), .Output(
    signextend_out));
52
53  and(and1_out, eBranch, ALU_zero); // and1 for beq
54  and(and2_out, nBranch, ~ALU_zero); // and2 for bne
55  or(or_out, and1_out, and2_out); // or for branch or not
56
57  initial begin #5 add_amount = 32'h4; end
58
59  // instruction decoding
60  assign ins_opcode = ins_out[31:26];
61  assign ins_rs = ins_out[25:21];
62  assign ins_rt = ins_out[20:16];
63  assign ins_rd = ins_out[15:11];
64  assign ins_funcnt = ins_out[5:0];
65  assign ins_imm = ins_out[15:0];
66  assign ins_except_op = ins_out[25:0];
67  assign jumpAddress = {add1_out[31:28], shift1_out};
68
69  endmodule

```


3.3 Simulation

We write several testbenches to test whether each module works well. After making sure that they all work well, we write the final testbench for **Top Module** in `test_single.v`. We use the MIPS instructions provided by TA to do the simulation.

3.3.1 Simulation Scenario

The content of the Instruction Memory used in this simulation is as follows:

```
memory[0] = 32'b00100000000010000000000000100000; //addi $t0, $zero, 0x20
memory[1] = 32'b00100000000010010000000000110111; //addi $t1, $zero, 0x37
memory[2] = 32'b0000000010000100110000000000100100; //and $s0, $t0, $t1
memory[3] = 32'b0000000010000100110000000000100101; //or $s0, $t0, $t1
memory[4] = 32'b101011000001000000000000000000100; //sw $s0, 4($zero)
memory[5] = 32'b1010110000001000000000000000001000; //sw $t0, 8($zero)
memory[6] = 32'b000000001000010011000100000100000; //add $s1, $t0, $t1
memory[7] = 32'b000000001000010011001000000100010; //sub $s2, $t0, $t1
memory[8] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[9] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[10] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[11] = 32'b000100100011001000000000000010010; //beq $s1, $s2, error0
memory[12] = 32'b100011000001000100000000000000100; //lw $s1, 4($zero)
memory[13] = 32'b0011001000110010000000000001001000; //andi $s2, $s1, 0x48
memory[14] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[15] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[16] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[17] = 32'b000100100011001000000000000001111; //beq $s1, $s2, error1
memory[18] = 32'b100011000001001100000000000001000; //lw $s3, 8($zero)
memory[19] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[20] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[21] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[22] = 32'b000100100001001100000000000001101; //beq $s0, $s3, error2
memory[23] = 32'b0000000100101000110100000000101010; //slt $s4, $s2, $s1 (Last)
memory[24] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[25] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[26] = 32'b001000000000100000000000000100000; //addi $t0, $zero, 0x20
memory[27] = 32'b000100101000000000000000000001111; //beq $s4, $0, EXIT
memory[28] = 32'b000000010001000001001000000100000; //add $s2, $s1, $0
memory[29] = 32'b0000100000000000000000000000010111; //j Last
memory[30] = 32'b001000000000100000000000000000000; //addi $t0, $0, 0(error0)
memory[31] = 32'b001000000000100100000000000000000; //addi $t1, $0, 0
memory[32] = 32'b0000100000000000000000000000011111; //j EXIT
memory[33] = 32'b001000000000100000000000000000001; //addi $t0, $0, 1(error1)
memory[34] = 32'b001000000000100100000000000000001; //addi $t1, $0, 1
```

```

memory[35] =32'b00001000000000000000000000000000111111; //j EXIT
memory[36] =32'b0010000000000100000000000000000010; //addi $t0, $0, 2(error2)
memory[37] =32'b0010000000000100100000000000000010; //addi $t1, $0, 2
memory[38] =32'b00001000000000000000000000000000111111; //j EXIT
memory[39] =32'b0010000000000100000000000000000011; //addi $t0, $0, 3(error3)
memory[40] =32'b0010000000000100100000000000000011; //addi $t1, $0, 3
memory[41] =32'b00001000000000000000000000000000111111; //j EXIT}

```

The code for testbench is shown in the Appendix section.

3.3.2 Textual Result

We use the command `iverilog -o test_single.vvp test_single.v` in terminal to compile the testbench, and then run the `test_single.vvp` file and redirect the result into `result.txt` file. The following shows the textual result before exiting the single cycle. **For the whole simulation result you can refer to section Appendix.**

```

[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
Time: 33, CLK = 1, PC = 0x00000068
[ $t0 ] = 0x00000020, [ $t1 ] = 0x00000037, [ $t2 ] = 0x00000000
[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
=====
Time: 34, CLK = 0, PC = 0x0000006c
[ $t0 ] = 0x00000020, [ $t1 ] = 0x00000037, [ $t2 ] = 0x00000000
[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
Time: 34, CLK = 1, PC = 0x0000006c
[ $t0 ] = 0x00000020, [ $t1 ] = 0x00000037, [ $t2 ] = 0x00000000
[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
=====
Time: 35, CLK = 0, PC = 0x000000ac
[ $t0 ] = 0x00000020, [ $t1 ] = 0x00000037, [ $t2 ] = 0x00000000
[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
Time: 35, CLK = 1, PC = 0x000000ac
[ $t0 ] = 0x00000020, [ $t1 ] = 0x00000037, [ $t2 ] = 0x00000000
[ $t3 ] = 0x00000000, [ $t4 ] = 0x00000000, [ $t5 ] = 0x00000000
[ $t6 ] = 0x00000000, [ $t7 ] = 0x00000000, [ $s0 ] = 0x00000037
[ $s1 ] = 0x00000037, [ $s2 ] = 0x00000037, [ $s3 ] = 0x00000020
[ $s4 ] = 0x00000000, [ $s5 ] = 0x00000000, [ $s6 ] = 0x00000000
[ $s7 ] = 0x00000000, [ $t8 ] = 0x00000000, [ $t9 ] = 0x00000000
Exit called

```

Figure 3: The simulation result before exit.

We can see that the result shown in Fig 3 accords the theoretical result. Our implementation of single cycle is successful.

4 Pipelined Implementation

4.1 Top Level Diagram

The top level diagram is as follows:

We provide a zoomed in image of each module below:

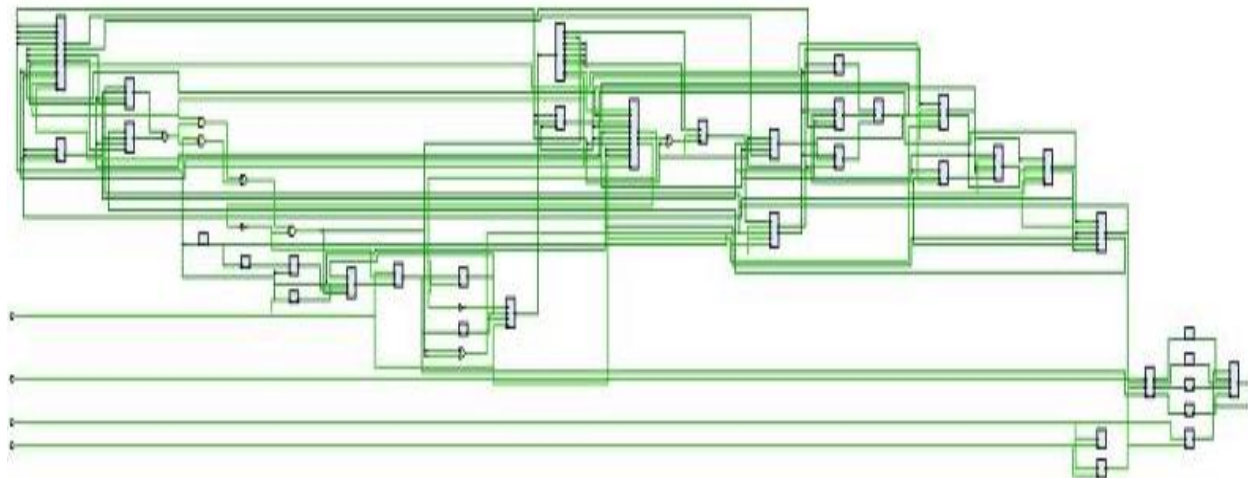


Figure 4: Top level diagram of pipelined implementation

 


Figure 5: Adder

 


Figure 6: ALU mux

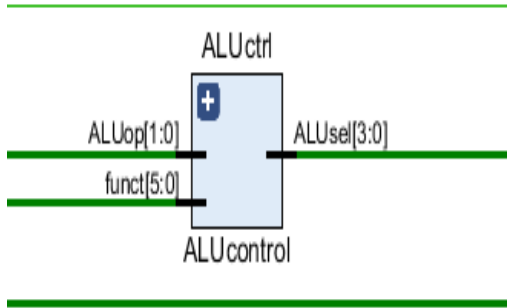


Figure 7: ALU Control

 


Figure 8: Data Memory

 


Figure 9: EX_regD1 mux

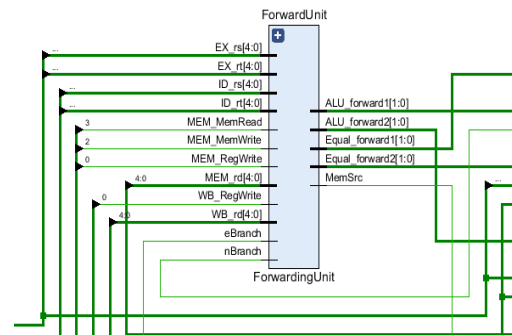


Figure 10: Forwarding Unit

 


Figure 11: HazardDetection

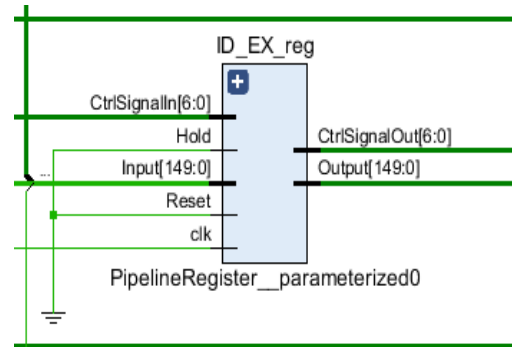


Figure 12: ID_EX pipelined register

 


Figure 13: 3 input mux

 


Figure 14: Instruction Memory

 


Figure 15: mux_control module

 


Figure 16: PC

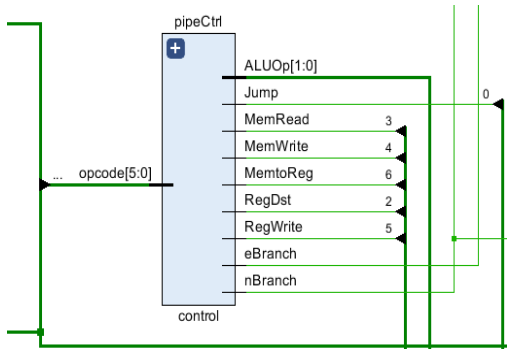


Figure 17: PipeCtrl module

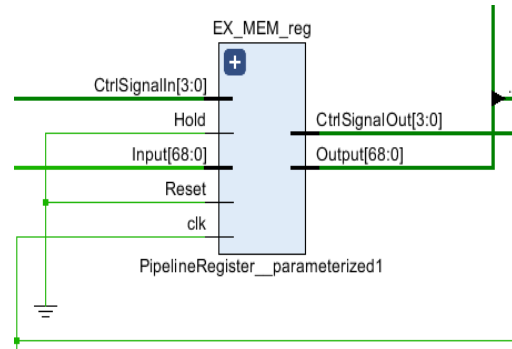


Figure 18: Pipeline Register

 


Figure 20: ShiftLeft2 module

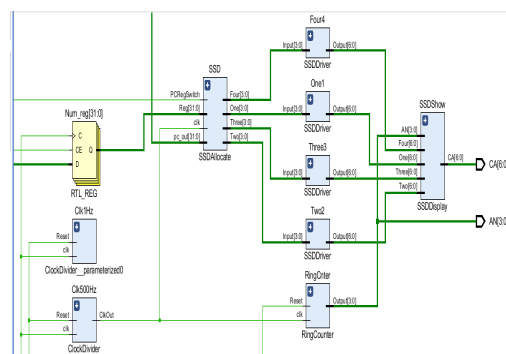


Figure 22: SSD module



4.2 Modules Design

There are 15 modules used in the pipelined design. The modules are: PC, ALU, ALU Control, Control, Adder, Data Memory, Instruction Memory, Mux(2 inputs and 3 inputs mux), Shift Left, Register File, Sign Extender, Forwarding Unit, Hazard Detection and Pipeline Register. The modules are put together in the Main module, which implements the pipelined MIPS computer. The implementation supports the following instructions: load word(lw), store word(sw), add, addi, sub, and, andi, or, slt, branch equal(beq), branch not equal(bne) and jump(j). This implementation takes on the **assume branch not taken** approach.

4.2.1 Components Design

PC module is used to generate the PC address. This module is written in the `pcPipeline.v` file. This PC module has an additional input `hold` from the one used in the single cycle implementation. `Hold` allows the PC to hold its PC value, such that it will only update the PC output if `Hold == 1`. The module is as follows:

```
1 module PC (pcAddrs, clock, outAddrs, hold);
2   input [31:0] pcAddrs; // Input address of PC
3   input clock, hold;    // Hold tells the PC whether to hold the address
4                       // or output the input address
5   output [31:0] outAddrs; // The output address of the PC
6
7   reg[31:0] pcReg;
8
9
10  initial begin
11    pcReg <= 32'b0;
12  end
13  assign outAddrs = pcReg;
14
15  always @(negedge clock) begin // PC updates at negedge clock
16    if(hold == 1'b0) begin
17      pcReg <= pcAddrs;
18    end
19  end
20
21 endmodule
22
23
24 endmodule
```


The ALU, ALU control, Adder, Data Memory, Instruction Memory, Mux (2 inputs), Shift Left, Register File and Sign Extender module is the same as the one used in the single cycle implementation. Please refer to the single cycle implementation Components Design section.

Mux (3 inputs) is just an upgrade from the 2 input mux. It is written in the Mux_3.v file. It takes three inputs (Input1, Input2, Input3) and a select signal (Selection). When Selection is 2'b00, the mux will output Input1. When Selection is 2'b01, the mux will output Input2. When Selection is 2'b10, the mux will output Input3. Else, it will output Input1 by default. Considering there are only 3 inputs, the Select should never be 2'b11. The Verilog code is as follows:

```

1
2 module Mux_3(
3 Selection,
4 Input1,
5 Input2,
6 Input3,
7 Output
8 );
9 //based on HU Jiaoyang 517370910140 2 input Mux module in VE370 Project 2 in
   19FA
10
11 parameter Digits = 32; //this is subject to change depending on which path this
   component is on
12 input [Digits-1:0] Input1, Input2, Input3;
13 output reg [Digits-1:0] Output;
14 input [1:0] Selection;
15
16 always @ (*) begin
17     if(Selection == 2'b00) begin Output <= Input1; end
18     else if(Selection == 2'b01) begin Output <= Input2; end
19     else if(Selection == 2'b10) begin Output <= Input3; end
20     else begin Output <= Input1; end
21 end
22 endmodule

```

4.2.2 Data Hazards Handling

Hazard Detection Unit is written in HazardDetection.v, mainly to deal with Load-use Hazard and Branch Hazard. The HazardDetection module has 11 inputs: clk, IDEXMemRead, Branch, nBranch, EXMEMMemRead, EXMEMRegWrite, IFIDRt, IFIDRs,

IDEXRt, EXMEMRt, EXMEMRd, and 3 output: PCWrite, IFIDWrite, MuxSelect. The module is synchronous, and works in ID stage of the processor. The module looks for data hazards that cannot be solved with forwarding (unlike EX/MEM hazards), and it inserts stalls into the processor to prevent the hazards from happening.

In the case of Load-use Hazard, the result of lw is obtained in the MEM stage of the instruction, however, the next instruction uses its result as either Rs or Rt, and require it in the EX stage. Therefore, the processor has to delay for one cycle before forwarding the result of lw from MEM/WB pipeline register to ID/EX pipeline register.

The way to detect Load-use Hazard is to first confirm that the first instruction is lw, which is to check IDEXMemRead. Next is to check that the result of lw is required in the next instruction, which is to check whether the Rt in the ID/EX pipeline register (executing lw instruction), is the same as either Rs or Rt in the next instruction's IF/ID pipeline register. Next is confirm that the next instruction is not branch instruction, because otherwise it would be a branch hazard, this is done by checking branch signal that we placed in the processor. After all is confirmed, we hold the processor by making PCWrite and IF/IDWrite 0, and select mux result to be 1, and flush the pipeline register.

A typical example of triggering the hazard looks like this:

```

1 addi $t0,$t0,6
2 addi $t1,$t1,16//address for $s0
3 sw $t0,$t1($zero)//store 6 in $s0
4 addi $t0,$zero,0
5 addi $t0,$zero,0//stalls
6 lw $t2,$t1($zero)//loading 6 from $s0 and place into $t2
7 add $t3,$t2,$t1//adding 6 in $t2, 16 in $t1 and place result into $t3

```

Translating these codes into machine code we get:

```

1 001000010000100000000000000000001110//addi $t0,$t0,6
2 0010000100101001000000000000000010000//addi $t1,$t1,16
3 101011010010100000000000000000000000//sw $t0,0($t1)
4 001000010000100000000000000000000000//addi $t0,$t0,0
5 001000010000100000000000000000000000//addi $t0,$t0,0
6 100011010010101000000000000000000000//lw $t2,0($t1)
7 00000001001010100101100000100000//add $t3,$t2,$t1

```

It should be straightforward that the result will be:

[\$t0] = 0,[\$t1] = 16,[\$t2] = 6,[\$t3] = 22. And after simulation, we see in the TCL Concole:

Exit called, executing final instructions

Final register state:

And after

[\$t0] = 0x00000006, [\$t1] = 0x00000010, [\$t2] = 0x00000006
[\$t3] = 0x00000016, [\$t4] = 0x00000000, [\$t5] = 0x00000000

We can see that the results are the same with what we expected, which indicate that we have successfully solved the Load-use Hazard.

In the case of Branch Hazards, there are a total of three instances that we need to consider.

Firstly, we need to consider the case in which `lw` is immediately followed by a branch instruction, like so:

```
1 //lw $1,addr
2 //beq $1,$0,target(Here we need to insert two bubbles)
```

Since a branch instruction requires its input in ID stage, and we can only obtain the result of `lw` in its MEM stage, we have to insert two stalls before the forwarding unit can send the result from the MEM/WB pipeline register of `lw` to the IF/ID register of branch.

We can identify this type of branch hazard by firstly confirming that the first signal is `lw`, which is checking ID/EXMemRead. After that we check the branch signal that it's branch, and then compare the `Rs,Rt` in branch with `Rt` in `lw` to confirm whether there is a hazard. Since we need to insert two bubbles, Hazard Detection Unit has a register called DoubleBubble. The register is changed to 1 when this instance of the branch hazard occurs. And in every clock cycle, the unit checks the DoubleBubble, and insert a second bubble when the value stored inside the register is 1.

The second instance is very similar to the first, in which an irrelevant instruction is inserted between `lw` and branch instruction, and we only need to insert one bubble.

Here's an instance of this type of branch hazard.

```
1 //lw $1,addr
2 //addi $2,$2,0
3 //beq $1,$0,target(Here we need to insert two bubbles)
```

The third instance is an R-type instruction followed by a branch instruction. The ID stage of branch instruction needs the output of the first instruction, which is not available until the EX stage of the first instruction. Therefore, the processor inserts one bubble, and after the bubble the forwarding unit can forward the result from EX/MEM pipeline register to ID stage.

To check for this type of hazard, we need to make sure the first instruction is not `lw`, which means checking that EXMEMRead is 0 and EXMEMRegWrite is 1. Next is checking that the second instruction is branch, which is done by checking the branch signal that we placed inside the processor. Finally, to confirm the hazard, we compare the `Rd` of the first instruction with the `Rs` and `Rt` of the branch instruction. With the above confirmed, we can safely say that there is the branch hazard, and we flush the pipeline registers and hold PC and IF/ID pipeline.

Here's an instance of this type of branch hazard.

```

1 //add $4,$5,$6
2 //beq $1,$4,target(Here we need to insert one bubble)

```

The Verilog code of **Hazard Detection Unit** is as follows:

```

1 `timescale 1ns / 100ps
2
3 module HazardDetection(
4   clk,
5   IDEXRt,
6   IFIDRt,
7   IFIDRs,
8   IFIDWrite,
9   PCWrite,
10  MuxSelect,
11  IDEXMemRead,
12  Branch,
13  nBranch,
14  EXMEMMemRead,
15  EXMEMRt,
16  EXMEMRd,
17  EXMEMRegWrite
18 );
19 //by HU Jiaoyang 517370910140 in VE370 19FA Project2
20 //we are checking data hazards that cannot be solved with forwarding(not like
    some data hazards)
21 //Therefore, this module adds bubbles who stalling the processor is the only
    solution
22 input  [4:0] IFIDRt,IFIDRs,IDEXRt,EXMEMRt,EXMEMRd;
23 input  clk, IDEXMemRead,Branch,nBranch,EXMEMMemRead,EXMEMRegWrite;
24 output reg PCWrite,IFIDWrite,MuxSelect;
25
26 reg DoubleBubble;
27 //We start by initializing the variables
28 initial begin
29   PCWrite <= 1'b1;
30   IFIDWrite <= 1'b1;
31   MuxSelect <= 1'b0;
32 end
33
34 //Sometimes we need to insert double bubble, so in this cycle we might need to
    continue inserting bubbles following the command from last cycle
35 always @ (posedge clk) begin
36   if(DoubleBubble == 1'b1) begin
37     DoubleBubble <= 1'b0;

```

```

38 PCWrite <= 1'b0;
39 IFIDWrite <= 1'b0;
40 MuxSelect <= 1'b1;
41 end
42 //Insert another bubble, reset the DoubleBubble variable
43
44 //Now after dealing with DoubleBubble issue, we now initialize the variable
    again before detecting hazards
45 else begin
46 DoubleBubble <= 1'b0;
47 PCWrite <= 1'b1;
48 IFIDWrite <= 1'b1;
49 MuxSelect <= 1'b0;
50 //Here we consider a Load-use hazard that also requires one stall
51 //Hazard 01
52 //lw $1,addr
53 //nop
54 //add $0,$1,$4(Here we need to insert one bubble)
55 //Here we just need to stall one cycle so the EX of add comes after MEM of lw
56 if (IDEXMemRead == 1'b1) begin
57 if((IFIDRs == IDEXRt || IFIDRt == IDEXRt) && !(Branch || nBranch))begin
58 DoubleBubble <= 1'b0;
59 PCWrite <= 1'b0;
60 IFIDWrite <= 1'b0;
61 MuxSelect <= 1'b1;
62 end
63 end
64 //Here we consider three instances of branch hazard
65 //Hazard 02
66 //lw $1,addr
67 //beq stalled
68 //beq stalled
69 //beq $1,$0,target(Here we need to insert two bubbles)
70 //beq reads its rt in ID stage, so we need to: 1. make sure that it is branch
    2. make sure ID of beq comes after the MEM of lw
71 if (IDEXMemRead == 1'b1) begin
72 if((IFIDRs == IDEXRt || IFIDRt == IDEXRt)&&(Branch || nBranch))begin
73 DoubleBubble <= 1'b1;
74 PCWrite <= 1'b0;
75 IFIDWrite <= 1'b0;
76 MuxSelect <= 1'b1;
77 end
78 end
79
80 //Hazard 03

```

```

81 //lw $1, addr
82 //...
83 //beq stalled
84 //beq $1,$4,target(Here we need to insert one bubble)
85 if(EXMEMMemRead && (IFIDRs == EXMEMRt || IFIDRt == EXMEMRt)&&(Branch ||
    nBranch))begin
86 DoubleBubble <= 1'b0;
87 PCWrite <= 1'b0;
88 IFIDWrite <= 1'b0;
89 MuxSelect <= 1'b1;
90 end
91
92 //Hazard 04
93 //add $4,$5,$6
94 //beq stalled
95 //beq $1,$4,target(Here we need to insert one bubble)
96 if (!EXMEMMemRead && EXMEMRegWrite && (Branch || nBranch) && (EXMEMRd ==
    IFIDRs || EXMEMRd == IFIDRt)) begin
97 DoubleBubble <= 1'b0;
98 PCWrite<=1'b0;
99 IFIDWrite<=1'b0;
100 MuxSelect <=1'b1;
101 end
102 end
103 end
104 endmodule

```

Forwarding Unit Module is designed to resolve the problem of data dependency. It is written in `ForwardingUnit.v` file, and is mainly designed to solve 5 kinds of data dependency, which are MEM/EX hazard, WB/EX hazard, beq/bne with R/I type instruction, beq/bne with R/I type and lw instruction, and instruction that writes into register file following with sw.

In this project, we just use the function of solving 3 kinds of data dependency, MEM/EX hazard, WB/EX hazard and instruction that writes into register file following with sw. The example for MEM/EX hazard is:

```

1 add $4,$5,$6
2 add $5,$4,$0 // here $4 is in data dependency (MEM/EX)

```

The example for WB/EX hazard is:

```

1 add $4,$5,$6
2 addi $6, $5, 0
3 add $5,$4,$0 // here $4 is in data dependency (WB/EX)

```

In our design, the calculated result of register \$4 from add \$4,\$5,\$6 in WB stage will be directly forward to one of the input of register file RegRead1 or RegRead2 in EX stage, depending on where we detect data hazard, at rd or rs. Especially our Forwarding Unit can solve WB/EX hazard only when MEM/EX hazard doesn't happen. Hence in the example below, forwarding for WB/EX hazard won't be triggered.

```
1 add $4,$5,$6
2 addi $4, $5, 0
3 add $5,$4,$0 // here $4 is in data dependency (MEM/EX)
```

The example for the hazard where instruction writing into register file following with sw:

```
1 add $4,$5,$6
2 sw $5,4($4) // here $4 is in data dependency
```

In our design, the result coming from add in WB stage will be directly forward to the input of memory file in MEM stage. The following is the Verilog code of **Forwarding Unit**:

```
1 module ForwardingUnit (
2     ALU_forward1,
3     ALU_forward2,
4     Equal_forward1,
5     Equal_forward2,
6     MemSrc,
7     MEM_rd,
8     WB_rd,
9     EX_rs,
10    EX_rt,
11    MEM_RegWrite,
12    WB_RegWrite,
13    MEM_MemRead,
14    MEM_MemWrite,
15    eBranch,
16    nBranch,
17    ID_rs,
18    ID_rt
19 );
20
21 input [4:0] MEM_rd, WB_rd, EX_rs, EX_rt, ID_rs, ID_rt;
22 input MEM_RegWrite, WB_RegWrite, MEM_MemRead, MEM_MemWrite, eBranch,
    nBranch;
23 output reg [1:0] ALU_forward1, ALU_forward2, Equal_forward1,
    Equal_forward2;
24 output reg MemSrc;
25
26 //initialize control signals
```

```

27  initial begin
28      ALU_forward1 <= 2'b00;
29      ALU_forward2 <= 2'b00;
30      Equal_forward1 <= 2'b00;
31      Equal_forward2 <= 2'b00;
32      MemSrc <= 1'b0;
33  end
34
35  always @ (*) begin
36      //default value
37      ALU_forward1 <= 2'b00;
38      ALU_forward2 <= 2'b00;
39      Equal_forward1 <= 2'b00;
40      Equal_forward2 <= 2'b00;
41      MemSrc <= 1'b0;
42      if (MEM_RegWrite == 1'b1) begin // For MEM hazard
43          if (MEM_rd == EX_rs) begin ALU_forward1 <= 2'b10;
44              $display("Forwarding_unit::_MEM/EX_hazard,_ForwardA_=_10");
45          end
46          if (MEM_rd == EX_rt) begin ALU_forward2 <= 2'b10;
47              $display("Forwarding_unit::_MEM/EX_hazard,_ForwardB_=_10");
48          end
49      end
50      if (WB_RegWrite == 1'b1) begin // For WB hazard
51          if (WB_rd == EX_rs && !(MEM_RegWrite == 1'b1 && MEM_rd == EX_rs))
52              begin ALU_forward1 <= 2'b01;
53                  $display("Forwarding_unit::_WB/EX_hazard,_ForwardA_=_01"); end
54          if (WB_rd == EX_rt && !(MEM_RegWrite == 1'b1 && MEM_rd == EX_rt))
55              begin ALU_forward2 <= 2'b01;
56                  $display("Forwarding_unit::_WB/EX_hazard,_ForwardA_=_01"); end
57      end
58      if (WB_RegWrite == 1'b1 && MEM_MemWrite == 1'b1) begin
59          // For sw immediately after operations that write in register file
60          if (WB_rd == MEM_rd) begin MemSrc <= 1'b1;
61              $display("Forwarding_unit::_WB/sw_hazard,_Forward_load_=_1"); end
62      end
63      if (WB_RegWrite == 1'b1 && (eBranch || nBranch)) begin
64          // For branch and lw/R/I type operation
65
66          if (WB_rd == ID_rs) begin Equal_forward1 <= 2'b01;
67              $display("Forwarding_unit::_WB/branch_hazard,_Forward_branch1_=_01");
68          end
69
70          if (WB_rd == ID_rt) begin Equal_forward2 <= 2'b01;

```



```

69         $display("Forwarding_unit::_WB/branch_hazard,_Forward_branch2=_01");
70         end
71     end
72     if (MEM_RegWrite == 1'b1 && (eBranch || nBranch) && MEM_MemRead == 1'b0)
73         begin
74             // For branch and R/I type operation (no lw)
75             if (MEM_rd == ID_rs) begin Equal_forward1 <= 2'b10;
76                 $display("Forwarding_unit::_MEM/branch_hazard,_Forward_branch1=_10");
77                 end
78             if (MEM_rd == ID_rt) begin Equal_forward2 <= 2'b10;
79                 $display("Forwarding_unit::_MEM/branch_hazard,_Forward_branch1=_01"); end
80             end
81         end
82     endmodule

```

4.2.3 Top Module Design

The top module of the pipelined MIPS computer is written in the `main_pipeline.v` file. In this implementation, the assume branch not taken approach was used, which means the pc will always increase by 4 and if a branch is taken (decided in the ID stage), the IF/ID pipeline registered will be flushed (all data set to 0 and all controls signals set to 0). The instruction supplied to the PC to be executed next will be the target address of the branch. In the IF stage, the main task being executed is choosing the correct PC address and fetching the instruction at that address from the Instruction Memory. A 3 input mux, `branch_mux` outputs either `PC + 4` (`PC_add4`), target address of the jump instruction (`jump_addrs`) or target address of branch instruction (`branch_addrs`). The output of the mux is called the `pc_addrs`, which will be the address sent to the Instruction Memory. The Instruction Memory, `insMem`, fetches the instruction from the address `pc_addrs` and outputs the instruction (`insmem_out`). The IF/ID pipeline register takes in the following inputs from the IF stage: `PC_add4`, `insmem_out` and outputs them as `ID_pc4`, `ins`.

The ID stage decodes the instruction in the IF/ID register into `ins_op` (`ins[31:26]`), `ins_rs` (`ins[25:21]`), `ins_rt` (`ins[20:16]`), `ins_rd` (`ins[15:11]`), `ins_funct` (`ins[5:0]`), `ins_imm` (`ins[15:0]`), `ins_jump` (`ins[25:0]`). The usage of each signal will be further explained. A control module, `pipeCtrl` is available in the ID stage, which takes it `ins_op` as input and outputs 9 control signals namely `ID_regDst`, `jump`, `Branch`, `nBranch`, `ID_memRead`, `ID_MemtoReg`, `ALUOp`, `ID_memWrite`, `ID_regWrite`. There is also a register file, `regFile`, in the ID stage. `in_rs` will always be connected to the `readRegister1` input and `in_rt`

will always be connected to the `readRegister2` input of the register file. When the `RegWrite` input of the register file is 1, it will write to the register. This input comes from the WB stage (`WB_regWrite`). The `writeData` and `writeRegister` inputs also come from the WB stage, which are `WB_data` and `WB_dest` respectively. Note that pipeline and pc is updated during negative edge of clock while information is written to register during the positive edge of clock.

The register file will then output the data from the register, namely `reg_D1` and `reg_D2`. The decision to branch is also made in this stage. It compares the two registers in the beq instruction with a comparator and outputs `equal = 1` if the data are equal, 0 otherwise. The forwarding and any possible hazards related to the input data and output data are dealt with by the Hazard Detection Unit and Forwarding Unit. If the instruction is a beq instruction, which means the Branch signal will be one, `branch_eq = 1` if `equal = 1`. For bne instruction, `branch_neq` will be 1 if `equal = 0`. This can be done by simple or & and logic gates. The wire that decides whether if a branch equal or branch not equal instruction will occur is the `final_branch` wire. A jump instruction is always executed. The branch and jump target addresses will be sent as the inputs of `branch_mux` in IF stage and the `{final_branch, jump}` signals will be the selection signal of the mux.

In the EX stage, the ALU executes the execution required by each instructions. The first input of the ALU (`ALU_in1`) comes from a mux which choose whether to output the value previously read from register (`EX_reg_D1`) or forwarded inputs from MEM or WB stage. For the second input of the ALU (`ALU_in2`), a mux similar to the one for the first input is also present. However, the output of this mux (`D2_m1_out`) serves as an input to another mux which chooses between this input or `EX_imm`, which is the extended immediate number. The control signals of the ALU comes from the ALU Control module, which is also present in the EX stage.

In the MEM stage, the main operation is done by the Data Memory module. If `MEM_memRead == 1` data is fetched from the memory at the address supplied by `MEM_ALUres`, which is the ALU result previously obtained in the EX stage. If (`MEM_memWrite == 1`), data is stored to that address. A mux is present to choose the write data. The data might come from either the output of the register file previously obtained in the ID stage and and stored in the ID/EX pipeline register or the data forwarded from the WB stage.

In the WB stage, the data is written back to the register if `WB_regWrite == 1`. A mux is present to choose the data to be written back. The data might either be from the output of the Data Memory in the previous stage, which is stored in the MEM/WB pipeline register

as WB_MEM_data , or from ALU result previously obtain in the EX stage, which is stored in the pipeline register as WB_reg_data. The signal controlling the mux is WB_MemtoReg.

The Verilog code of the main module is as follows:

```

1
2 //2019 Fall VE370 project 2 Group 32, main module by: Gracia Stefani
   517370990022
3 //This module assumes branch is not taken
4 `include "ShiftLeft2.v"
5 `include "Mux.v"
6 `include "Adder.v"
7 `include "SignExtend.v"
8 `include "InstructionMemory.v"
9 `include "ALU.v"
10 `include "pcPipeline.v"
11 `include "dataMem.v"
12 `include "Control.v"
13 `include "ALUcontrol.v"
14 `include "RegisterFile.v"
15 `include "PipelineRegister.v"
16 `include "HazardDetection.v"
17 `include "ForwardingUnit.v"
18 `include "Mux_3.v"
19
20 module main(clk);
21
22     input clk;
23
24     //declaration of wires
25     wire [31:0] pc_out, insmem_out, ins, reg_D1, reg_D2, comp_1, comp_2,
        ins_imm_ext,ins_sh_emm, ID_pc4,jump_addrs, PC_add4, pc_addrs,branch_addrs
        ,EX_imm, EX_reg_D2, EX_reg_D1,ALU_in1, ALU_in2, D2_m1_out, ALU_res,
        MEM_D1, MEM_ALUres, MEM_WD, MEM_readData, WB_MEM_data, WB_reg_data,
        WB_data , EX_pc4, branch_mux_out;
26     wire [4:0] ins_rs, ins_rt, ins_rd,EX_rs, EX_rt, EX_rd, EX_dest, MEM_dest,
        WB_dest;
27     wire [5:0] ins_op, ins_funcnt, EX_funcnt;
28     wire [25:0] ins_jump;
29     wire [15:0] ins_imm;
30     wire [27:0] ins_sh_out;
31     wire IF_hold, PC_hold, Bubble, MEM_memRead, MEM_MemtoReg, MEM_memWrite,
        go_branch, jump, IF_flush, EX_flush, branch_neq, branch_eq, nBranch,
        Branch, WB_MemtoReg, WB_regWrite, Forward_load, ID_regDst, ID_memWrite,
        ID_MemtoReg, ID_memRead, ID_regWrite, equal, EX_memWrite, EX_MemtoReg,
        EX_regDst, EX_memRead, EX_regWrite, zero, BubCtrl, final_branch, nothing1,

```

```

nothing2, BubCheck, or_branch, or_JB, branch_xnor, branch_check,
flush_check, jump_check, IF_Write, PC_Write; //BubCheck sets the value of
BubCtrl to 0 if EX_flush is x
32 wire [1:0] ALUop, EX_ALUop, ForwardA, ForwardB, Forward_branch1,
Forward_branch2;
33 wire [3:0] ALU_control;
34 wire [6:0] control_out;
35
36 //declaration of modules
37
38 Adder pcAdd (.Input1(pc_out), .Input2(32'h4), .Output(PC_add4));
39 Adder branchAdd (.Input1(ins_sh_emm), .Input2(ID_pc4), .Output(branch_addrs)
);
40 ALU MEM_ALU (.in1(ALU_in1), .in2(ALU_in2), .control(ALU_control), .zero(zero
), .aluRes(ALU_res));
41 ALUcontrol ALUctrl(.ALUop(EX_ALUop), .funct(EX_funct), .ALUsel(ALU_control))
;
42 dataMem dataMemory (.clock(clk), .memRead(MEM_memRead), .memWrite(
MEM_memWrite), .address(MEM_ALUres), .wData(MEM_WD), .rData(MEM_readData)
);
43 InstructionMemory insMem (.Address(pc_out), .Instruction(insmem_out));
44
45 control pipeCtrl (.opcode(ins_op), .RegDst(ID_regDst), .Jump(jump), .eBranch
(Branch), .nBranch(nBranch), .MemRead(ID_memRead), .MemtoReg(ID_MemtoReg)
, .ALUOp(ALUop), .MemWrite(ID_memWrite), .RegWrite(ID_regWrite));
46
47 Mux #(.Digits(7)) mux_control (.Selection(BubCtrl), .Input1({ID_MemtoReg,
ID_regWrite, ID_memWrite, ID_memRead, ID_regDst, ALUop}), .Input2(7'b0), .
Output(control_out));
48 Mux #(.Digits(5)) mux_dest (.Selection(EX_regDst), .Input1(EX_rt), .Input2(
EX_rd), .Output(EX_dest));
49 Mux MEM_mux (.Selection(Forward_load), .Input1(MEM_D1), .Input2(WB_data), .
Output(MEM_WD));
50 Mux WB_mux (.Selection(WB_MemtoReg), .Input1(WB_reg_data), .Input2(
WB_MEM_data), .Output(WB_data));
51 Mux ALU_mux (.Selection(EX_regDst), .Input1(EX_imm), .Input2(D2_m1_out), .
Output(ALU_in2));
52
53 Mux_3 branch_mux (.Selection({branch_check, jump_check}), .Input1(PC_add4), .
Input2(jump_addrs), .Input3(branch_addrs), .Output(pc_addrs));
54 //Mux pc_mux (.Selection(flush_check), .Input1(branch_mux_out), .Input2(
ID_pc4), .Output(pc_addrs));
55 Mux_3 regD1_mux (.Selection(Forward_branch1), .Input1(reg_D1), .Input3(
MEM_ALUres), .Input2(WB_data), .Output(comp_1));
56 Mux_3 regD2_mux (.Selection(Forward_branch2), .Input1(reg_D2), .Input3(

```

```

MEM_ALUres), .Input2(WB_data), .Output(comp_2));
57 Mux_3 EX_regD1_mux (.Selection(ForwardA), .Input1(EX_reg_D1), .Input3(
    MEM_ALUres), .Input2(WB_data), .Output(ALU_in1));
58 Mux_3 EX_regD2_mux (.Selection(ForwardB), .Input1(EX_reg_D2), .Input3(
    MEM_ALUres), .Input2(WB_data), .Output(D2_m1_out));
59
60 PC pc (.pcAddr(pc_addrs), .clock(clk), .outAddr(pc_out), .hold(PC_hold));
61 RegisterFile regFile (.clk(clk), .RegWrite(WB_regWrite), .readRegister1(
    ins_rs), .readRegister2(ins_rt), .writeRegister(WB_dest), .writeData(
    WB_data), .readData1(reg_D1), .readData2(reg_D2));
62
63 ShiftLeft2 branchSh (.Input(ins_imm_ext), .ShiftedOutput(ins_sh_emm));
64 ShiftLeft2 #(.Digits(28)) jumpSh (.Input({2'b0,ins_jump}), .ShiftedOutput(
    ins_sh_out));
65 SignExtend ext (.Input(ins_imm), .Output(ins_imm_ext));
66
67 and (branch_eq, Branch, equal);
68 and (branch_neq, nBranch, ~equal);
69 or (go_branch, branch_eq, branch_neq);
70 and (final_branch, go_branch, ~PC_hold);
71 or (IF_flush, final_branch, jump);
72 or(BubCtrl, Bubble, BubCheck); //if the IF/ID register is to be flushed,
    control signals should also be flushed, pass this flush control signal to
    EX stage since decision is available to be passed before the instruction
    to be flushed move to ID stage
73
74 PipelineRegister #(.Digits(64), .CtrlDigits(1)) IF_ID_reg (.clk(clk), .Input
    ({PC_add4, insmem_out}), .Output({ID_pc4,ins}), .CtrlSignalIn(nothing1),
    .CtrlSignalOut(nothing2) ,.Hold(IF_hold), .Reset(IF_flush));
75
76 PipelineRegister #(.Digits(150), .CtrlDigits(7)) ID_EX_reg (.clk(clk), .
    Input({reg_D1,reg_D2, ins_rs, ins_rt, ins_rd, ins_funcnt, ins_imm_ext,
    IF_flush, ID_pc4}), .Output({EX_reg_D1, EX_reg_D2, EX_rs, EX_rt, EX_rd,
    EX_funcnt, EX_imm, EX_flush, EX_pc4}), .CtrlSignalIn(control_out), .
    CtrlSignalOut({EX_MemtoReg, EX_regWrite,EX_memWrite, EX_memRead,EX_regDst
    , EX_ALUop}), .Hold(1'b0), .Reset(1'b0));
77
78 PipelineRegister #(.Digits(69), .CtrlDigits(4)) EX_MEM_reg (.clk(clk), .
    Input({ALU_res, D2_m1_out, EX_dest}), .Output({MEM_ALUres, MEM_D1,
    MEM_dest}), .CtrlSignalIn({EX_memRead, EX_memWrite, EX_MemtoReg,
    EX_regWrite}), .CtrlSignalOut({MEM_memRead, MEM_memWrite, MEM_MemtoReg,
    MEM_regWrite}), .Hold(1'b0), .Reset(1'b0));
79
80 PipelineRegister #(.Digits(69), .CtrlDigits(2)) MEM_WB_reg (.clk(clk), .
    Input({MEM_readData, MEM_ALUres, MEM_dest}), .Output({WB_MEM_data,

```

```

WB_reg_data, WB_dest}}, .CtrlSignalIn({MEM_MemtoReg, MEM_regWrite}), .
CtrlSignalOut({WB_MemtoReg, WB_regWrite}), .Hold(1'b0), .Reset(1'b0));
81
82 HazardDetection HazardD (.PCWrite(PC_Write), .IFIDWrite(IF_Write), .
MuxSelect(Bubble), .IDEXMemRead(EX_memRead), .EXMEMMemRead(MEM_memRead),
.Branch(Branch), .nBranch(nBranch), .IFIDRs(ins_rs), .IFIDRt(ins_rt), .
IDEXRt(EX_rt), .EXMEMRegWrite(EX_regWrite), .EXMEMRt(MEM_dest), .EXMEMRd(
EX_dest), .clk(clk));
83
84 ForwardingUnit ForwardUnit ( .ALU_forward1(ForwardA), .ALU_forward2(ForwardB
), .Equal_forward1(Forward_branch1), .Equal_forward2(Forward_branch2), .
MemSrc(Forward_load), .MEM_RegWrite(MEM_regWrite), .WB_RegWrite(
WB_regWrite), .MEM_rd(MEM_dest), .WB_rd(WB_dest), .EX_rs(EX_rs), .EX_rt(
EX_rt), .MEM_MemRead(MEM_memRead), .MEM_MemWrite(MEM_memWrite), .eBranch(
Branch), .nBranch(nBranch), .ID_rs(ins_rs), .ID_rt(ins_rt));
85
86 assign ins_op = ins[31:26];
87 assign ins_rs = ins[25:21];
88 assign ins_rt = ins[20:16];
89 assign ins_imm = ins[15:0];
90 assign ins_rd = ins[15:11];
91 assign ins_funct = ins[5:0];
92 assign ins_jump = ins[25:0];
93 assign equal = (comp_1 == comp_2) ? 1 : 0;
94 assign jump_addrs = {ID_pc4[31:28], ins_sh_out};
95 assign PC_hold = ~PC_Write;
96 assign IF_hold = ~ IF_Write;
97
98 //Allows initialization of necessary control signals to 0
99 assign BubCheck = (EX_flush === 1'bx) ? 0 : EX_flush;
100 assign flush_check = (IF_flush === 1'bx) ? 0 : IF_flush;
101 assign branch_check = (final_branch === 1'bx) ? 0 : final_branch;
102 assign jump_check = (jump === 1'bx) ? 0 : jump;
103 endmodule

```

4.3 Simulation

4.3.1 Simulation Scenario

The content of the Instruction Memory used in this simulation is as follows:

```

memory[0] = 32'b0010000000000100000000000001000000; //addi $t0, $zero, 0x20
memory[1] = 32'b0010000000000100100000000000110111; //addi $t1, $zero, 0x37
memory[2] = 32'b0000000010000100110000000000100100; //and $s0, $t0, $t1
memory[3] = 32'b0000000010000100110000000000100101; //or $s0, $t0, $t1

```

```

memory[4] = 32'b10101100000010000000000000000000100; //sw $s0, 4($zero)
memory[5] = 32'b101011000000010000000000000000001000; //sw $t0, 8($zero)
memory[6] = 32'b0000000010000100110001000000100000; //add $s1, $t0, $t1
memory[7] = 32'b0000000010000100110010000000100010; //sub $s2, $t0, $t1
memory[8] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[9] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[10] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[11] = 32'b0001001000110010000000000000010010; //beq $s1, $s2, error0
memory[12] = 32'b1000110000001000100000000000000100; //lw $s1, 4($zero)
memory[13] = 32'b0011001000110010000000000001001000; //andi $s2, $s1, 0x48
memory[14] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[15] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[16] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[17] = 32'b0001001000110010000000000000001111; //beq $s1, $s2, error1
memory[18] = 32'b10001100000010011000000000000001000; //lw $s3, 8($zero)
memory[19] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[20] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[21] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[22] = 32'b0001001000010011000000000000001101; //beq $s0, $s3, error2
memory[23] = 32'b0000000100101000110100000000101010; //slt $s4, $s2, $s1 (Last)
memory[24] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[25] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[26] = 32'b00100000000001000000000000000100000; //addi $t0, $zero, 0x20
memory[27] = 32'b0001001010000000000000000000001111; //beq $s4, $0, EXIT
memory[28] = 32'b00000001000100000010010000000100000; //add $s2, $s1, $0
memory[29] = 32'b00001000000000000000000000000010111; //j Last
memory[30] = 32'b0010000000000100000000000000000000; //addi $t0, $0, 0(error0)
memory[31] = 32'b0010000000000100100000000000000000; //addi $t1, $0, 0
memory[32] = 32'b000010000000000000000000000000111111; //j EXIT
memory[33] = 32'b0010000000000100000000000000000001; //addi $t0, $0, 1(error1)
memory[34] = 32'b0010000000000100100000000000000001; //addi $t1, $0, 1
memory[35] = 32'b000010000000000000000000000000111111; //j EXIT
memory[36] = 32'b0010000000000100000000000000000010; //addi $t0, $0, 2(error2)
memory[37] = 32'b0010000000000100100000000000000010; //addi $t1, $0, 2
memory[38] = 32'b000010000000000000000000000000111111; //j EXIT
memory[39] = 32'b0010000000000100000000000000000011; //addi $t0, $0, 3(error3)
memory[40] = 32'b0010000000000100100000000000000011; //addi $t1, $0, 3
memory[41] = 32'b000010000000000000000000000000111111; //j EXIT}

```

4.3.2 Textual Result

```
Time: 28, Clock = 0, PC = 0x0000006c
Instruction fetched = 000100101000000000000000001111
Instruction in IF/ID register = 001000000001000000000000100000
Control signals in IF/ID stage = 0100000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 28, Clock = 1, PC = 0x0000006c
Instruction fetched = 000100101000000000000000001111
Instruction in IF/ID register = 001000000001000000000000100000
Control signals in IF/ID stage = 0100000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 29, Clock = 0, PC = 0x00000070
Instruction fetched = 00000010001000001001000000100000
Instruction in IF/ID register = 000100101000000000000000001111
Control signals in IF/ID stage = 0000001
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 29, Clock = 1, PC = 0x00000070
Instruction fetched = 00000010001000001001000000100000
Instruction in IF/ID register = 000100101000000000000000001111
Control signals in IF/ID stage = 0000001
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000
```

Figure 24: State of registers at time = 28

The instruction at 0x0000006c is beq \$s4, 0, EXIT. Since this implementation assumes branch not taken, the PC will still increment by 4 after fetching the beq instruction. When PC = 0x00000070, it is able to decide that branch is not taken since \$s4 = 0x00000001, so it doesn't have to take any penalty.

```
*****
Time: 30, Clock = 0, PC = 0x00000074
Instruction fetched = 0000100000000000000000000010111
Instruction in IF/ID register = 00000010001000001001000000100000
Control signals in IF/ID stage = 0100110
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 30, Clock = 1, PC = 0x00000074
Instruction fetched = 0000100000000000000000000010111
Instruction in IF/ID register = 00000010001000001001000000100000
Control signals in IF/ID stage = 0100110
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 31, Clock = 0, PC = 0x00000078
Instruction fetched = 00100000000010000000000000000000
Instruction in IF/ID register = 0000100000000000000000000010111
Control signals in IF/ID stage = 0000000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 31, Clock = 1, PC = 0x00000078
Instruction fetched = 00100000000010000000000000000000
Instruction in IF/ID register = 0000100000000000000000000010111
Control signals in IF/ID stage = 0000000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000
```

Figure 25: State of registers at time = 30

```

*****
Time: 32, Clock = 0, PC = 0x0000005c
Instruction fetched = 00000010010100011010000000101010
Instruction in IF/ID register = 00000000000000000000000000000000
Control signals in IF/ID stage = 0000000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

Branch taken, IF/ID register flushed.

*****
Time: 32, Clock = 1, PC = 0x0000005c
Instruction fetched = 00000010010100011010000000101010
Instruction in IF/ID register = 00000000000000000000000000000000
Control signals in IF/ID stage = 0000000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000000, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

```

Figure 26: State of registers at time = 32

The instruction at 0x00000074 is j Last. Here, branch is taken, thus the IF/ID register has to be flushed. As can be seen, it will jump to 0x0000005c after it realizes that branch should be taken, which takes one clock cycle from the time the instruction is fetched. Since branch was taken, it flushed the IF/ID register containing the instruction at 0x00000078. It can be seen that the register has been flushed successfully since the instruction in the register is 32'b0 and control signals to be passed to ID/EX register is 7'b0.

```

*****
Time: 36, Clock = 0, PC = 0x000006c
Instruction fetched = 000100101000000000000000001111
Instruction in IF/ID register = 0010000000001000000000000100000
Control signals in IF/ID stage = 0100000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000001, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 36, Clock = 1, PC = 0x000006c
Instruction fetched = 000100101000000000000000001111
Instruction in IF/ID register = 0010000000001000000000000100000
Control signals in IF/ID stage = 0100000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 37, Clock = 0, PC = 0x0000070
Instruction fetched = 00000010001000001001000000100000
Instruction in IF/ID register = 000100101000000000000000001111
Control signals in IF/ID stage = 0000001
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

```

Figure 27: State of registers at time = 36

```

*****
Time: 37, Clock = 1, PC = 0x0000070
Instruction fetched = 00000010001000001001000000100000
Instruction in IF/ID register = 000100101000000000000000001111
Control signals in IF/ID stage = 0000001
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

*****
Time: 38, Clock = 0, PC = 0x00000ac
Instruction fetched = xxxxxxxxxxxxxxxxxxxxxxxxxxxxxxxx
Instruction in IF/ID register = 000000000000000000000000000000
Control signals in IF/ID stage = 0000000
[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

Branch taken, IF/ID register flushed.

Exit called, executing final instructions
Final register state:

[$t0] = 0x00000020, [$t1] = 0x00000037, [$t2] = 0x00000000
[$t3] = 0x00000000, [$t4] = 0x00000000, [$t5] = 0x00000000
[$t6] = 0x00000000, [$t7] = 0x00000000, [$s0] = 0x00000037
[$s1] = 0x00000037, [$s2] = 0x00000037, [$s3] = 0x00000020
[$s4] = 0x00000000, [$s5] = 0x00000000, [$s6] = 0x00000000
[$s7] = 0x00000000, [$t8] = 0x00000000, [$t9] = 0x00000000

```

Figure 28: Final state of register

At Time = 36, the instruction fetches the beq \$s4, 0, EXIT at 0x0000006c for the second time. However this time, it is supposed to jump since \$s4 should be 0. Note that the pipeline registers and PC are updated at negative edge of clock while the registers are updated as positive edge of clock, hence \$s4 changes at positive edge of clock in the graph above.

As expected, at Time = 37 it realizes that branch was taken, thus it sets the IF/ID register to be flushed at the next clock cycle and sends the instruction to branch in the next clock cycle. Thus, at Time = 38, the IF/ID register containing the instruction at 0x00000070 is flushed and the PC address is the target address of the branch instruction. The final state of the register after executing the remaining instruction in EX, MEM, and WB stages is also shown.

Please view the Appendix section for the full textual result

4.4 FPGA Board Implementation

To implement the pipeline processor on the board, the first thing is to write SSD display modules to display the lower four hexadecimal digits of the output of program counter or any register file.

SSD is written in `SSDDisplay.v`, `SSDDriver.v`, `SSDAllocate.v`, `RingCounter.v`, `ClockDivider.v`. These modules work together to display the address from program counter, and the values in any register file.

In the top module we need to define these things: `PCRegSwitch`, `RegLocation`, `Portclk`. We write a sections of codes in main to access the content of the registers. The location of the register is indicated by the input `RegLocation`. We have a total of 18 registers whose content we may change, therefore, we used five switches to input the location of register whose values we wish to read, and they combine into one input `RegLocation`.

Next is to choose to either display PC or register file. `SSD Allocate` reads the input `PCRegSwitch`, and decides which should be the output.

Finally, the modules generates output onto SSD. The port clock is connected to W5 of the FPGA board, which has $100MHz$ frequency. We then use the clockdivider to make it into frequency $500Hz$, which is used to turn the AN so we can show all four numbers. We can show on SSD four hexadecimal digits at a time. `SSD Driver` can transform the four digits from either PC or register into four 7-bit variable which can be used to control cathodes in SSD. `SSD Display` and `RingCounter` are the modules that control the anodes, and they work with the rest of the modules to show the digits.

The codes in The Verilog code is as follows:

ClockDivider.v

```

1 `timescale 1ns / 100ps
2
3 module ClockDivider#(
4     parameter Width = 3, // Width of the register required
5     parameter N = 6// We will divide by 12 for example in this case
6 )
7 (clk,Reset, ClkOut);
8 //By HU Jiaoyang 517370910140 at VE370 Project 2 19FA
9 input clk;
10 input Reset;
11 output ClkOut;
12
13 reg [Width-1:0] RReg;
14 wire [Width-1:0] RNext;
15 reg tmp;
16
17 always @(posedge clk or posedge Reset)
18
19 begin
20     if (Reset)
21         begin
22             RReg <= 0;
23             tmp <= 1'b0;
24         end
25
26         else if (RNext == N)
27             begin
28                 RReg <= 0;
29                 tmp <= ~tmp;
30             end
31
32         else
33             RReg <= RNext;
34 end
35
36 assign RNext = RReg + 1;
37 assign ClkOut = tmp;
38 endmodule

```

RingCounter.v

```

1 `timescale 1ns / 100ps
2
3 module RingCounter(
4     clk,

```

```

5 Reset,
6 Output
7 );
8 //by HU Jiaoyang VE370 Project 2 19FA
9 input clk,Reset;
10 output reg [3:0] Output;
11
12 always @ (posedge clk or posedge Reset) begin
13     if(Reset) Output <= 4'b1110;
14     else begin
15         Output[3] <= Output[0];
16         Output[2] <= Output[3];
17         Output[1] <= Output[2];
18         Output[0] <= Output[1];
19     end
20 end
21 endmodule

```

SSDAllocate.v

```

1 `timescale 1ns / 100ps
2 module SSDAllocate(
3 clk,PCRegSwitch,pc_out,Reg,Four,Three,Two,One
4 );
5     input clk,PCRegSwitch;
6     input [31:0] pc_out,Reg;
7     output reg [3:0] Four,Three,Two,One;
8     always @ (clk) begin
9         if (PCRegSwitch)begin
10             Four <= pc_out[15:12];
11             Three <= pc_out[11:8];
12             Two <= pc_out[7:4];
13             One <= pc_out[3:0];
14         end
15         else begin
16             Four <= Reg[15:12];
17             Three <= Reg[11:8];
18             Two <= Reg[7:4];
19             One <= Reg[3:0];
20         end
21     end
22 endmodule

```

SSDDisplay.v

```

1 `timescale 1ns / 100ps
2

```

```

3 module SSDDisplay(
4   input [6:0] Four,
5   input [6:0] Three,
6   input [6:0] Two,
7   input [6:0] One,
8   input [3:0] AN,
9   output [6:0] CA
10  );
11  //By HU Jiaoyang 517370910140 at VE370 Project 2 19FA
12  assign CA = (AN == 4'b1110) ? One : 7'bzzzzzzz,
13  CA = (AN == 4'b1101) ? Two : 7'bzzzzzzz,
14  CA= (AN == 4'b1011) ? Three : 7'bzzzzzzz,
15  CA = (AN == 4'b0111) ? Four : 7'bzzzzzzz;
16 endmodule

```

SSDDriver.v

```

1 `timescale 1ns / 100ps
2
3 module SSDDriver(
4   input [3:0] Input,
5   output reg [6:0] Output
6   );
7  //by HU Jiaoyang at 19FA VE370 Project 2
8  always @ (Input) begin
9      case(Input)
10         0: Output <= 7'b0000001;
11         1: Output <= 7'b1001111;
12         2: Output <= 7'b0010010;
13         3: Output <= 7'b0000110;
14         4: Output <= 7'b1001100;
15         5: Output <= 7'b0100100;
16         6: Output <= 7'b0100000;
17         7: Output <= 7'b0001111;
18         8: Output <= 7'b0000000;
19         9: Output <= 7'b0000100;
20         10: Output <= 7'b0001000;
21         11: Output <= 7'b1100000;
22         12: Output <= 7'b0110001;
23         13: Output <= 7'b1000010;
24         14: Output <= 7'b0110000;
25         15: Output <= 7'b0111000;
26         default Output <= 7'b1111111; // When there is no input, show nothing
27     endcase
28 end
29 endmodule

```

With SSD display finished, the next issue is I/O planning. Anodes(W4,V4,U4,U2) and cathodes(W7,W6,U8,V8,U5,V5,U7) of the SSD are connected to AN,CA of the program as output. As for the input, the pipeline processor takes the following inputs: clk, Port-clk,PCRegSwitch,Reset,RegLocation.clk is the switch that we are using as clock cycle input, therefore it is connected to V17 of the FPGA board.PCRegSwitch is the switch that decides whether SSD outputs the content of register file or the output of the program counter, we connect it to switch V16.RegLocation is a 5-bit input from switches that tells the processor to access $\$t0 - \$t9$ and $\$s0 - \$s7$. We connect the Reglocation to R2,T1,V1,W2,R3. We connect reset to button U18. To make SSD work, we need a clock to switch between the anodes and update the SSDs. Therefore, we take in the $100MHz$ clock from pin W5, and use clock divider to make it to $500Hz$.

5 Conclusion & Discussion

In this project, we successfully provided single cycle implementation and pipelined implementation for MIPS instruction. We tested our correctness by writing testbenches and compare the result of simulation with the theoretical ones. For pipelined implementation, we also run the program on FPGA board to check the value of registers after each clock cycle. We get to know all the details of how to implement hardware for MIPS computer, and understand the knowledge we have learned in class much better.

At first we have encountered with problems. When implementing single cycle case, we first run into the situation where the pc result is always 0xxxxxxxxx. After careful debugging we found that the error came from no delay of pc assignment. Hence we change the assignment style in **PC module** from "`<=`" to "`=`" to fix this problem.

After solving all those problems in the project, we learn more about how to deal with imperfectness in the real world, and grasp the theory better.

6 References

1. Patterson and Hennessy, Morgan Kaufmann Publishers, Computer Organization and Design.